

EXPT.-07

AIM: - Design and Simulate Up Counter using Verilog HDL.

Software: - Xilinx Vivado 2019.1

Theory: -


Counter is a sequential circuit. A digital circuit which is used for a counting pulses is known counter. Counter is the widest application of flip-flops. It is a group of flip-flops with a clock signal applied. Counters are of two types.

- Asynchronous or ripple counters.
- Synchronous counters.

Asynchronous or ripple counters

The logic diagram of a 2-bit ripple up counter is shown in figure. The toggle (T) flip-flop are being used. But we can use the JK flip-flop also with J and K connected permanently to logic 1. External clock is applied to the clock input of flip-flop A and Q_A output is applied to the clock input of the next flip-flop i.e. FF-B.

Logical Diagram

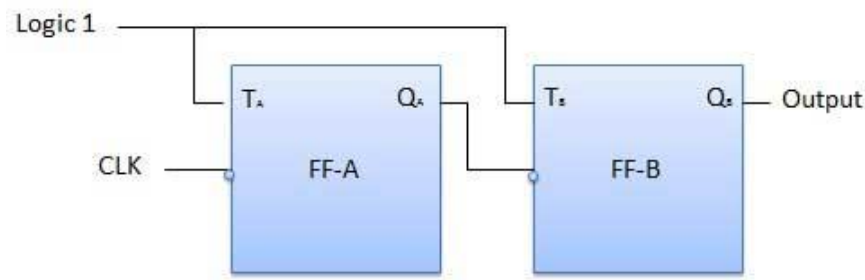

Operation

S.N.	Condition	Operation
1	Initially let both the FFs be in the reset state	$Q_B Q_A = 00$ initially
2	After 1st negative clock edge	As soon as the first negative clock edge is applied, FF-A will toggle and Q_A will be equal to 1.

		<p>Q_A is connected to clock input of FF-B. Since Q_A has changed from 0 to 1, it is treated as the positive clock edge by FF-B. There is no change in Q_B because FF-B is a negative edge triggered FF.</p> <p>$Q_B Q_A = 01$ after the first clock pulse.</p>
3	After 2nd negative clock edge	<p>On the arrival of second negative clock edge, FF-A toggles again and $Q_A = 0$.</p> <p>The change in Q_A acts as a negative clock edge for FF-B. So it will also toggle, and Q_B will be 1.</p> <p>$Q_B Q_A = 10$ after the second clock pulse.</p>
4	After 3rd negative clock edge	<p>On the arrival of 3rd negative clock edge, FF-A toggles again and Q_A become 1 from 0.</p> <p>Since this is a positive going change, FF-B does not respond to it and remains inactive. So Q_B does not change and continues to be equal to 1.</p> <p>$Q_B Q_A = 11$ after the third clock pulse.</p>
5	After 4th negative clock edge	<p>On the arrival of 4th negative clock edge, FF-A toggles again and Q_A becomes 0 from 1.</p> <p>This negative change in Q_A acts as clock pulse for</p>

FF-B. Hence it toggles to change Q_B from 1 to 0.

$Q_B Q_A = 00$ after the fourth clock pulse.

Truth Table

Clock	Counter output		State number	Decimal Counter output
	Q_B	Q_A		
Initially	0	0	—	0
1st	0	1	1	1
2nd	1	0	2	2
3rd	1	1	3	3
4th	0	0	4	0


Synchronous counters

If the "clock" pulses are applied to all the flip-flops in a counter simultaneously, then such a counter is called as synchronous counter.

2-bit Synchronous up counter

The J_A and K_A inputs of FF-A are tied to logic 1. So FF-A will work as a toggle flip-flop. The J_B and K_B inputs are connected to Q_A .

Logical Diagram

 

Operation

S.N.	Condition	Operation
1	Initially let both the FFs be in the reset state	$Q_B Q_A = 00$ initially.
2	After 1st negative clock edge	<p>As soon as the first negative clock edge is applied, FF-A will toggle and Q_A will change from 0 to 1.</p> <p>But at the instant of application of negative clock edge, $Q_A, J_B = K_B = 0$. Hence FF-B will not change its state. So Q_B will remain 0.</p> <p>$Q_B Q_A = 01$ after the first clock pulse.</p>
3	After 2nd negative clock edge	<p>On the arrival of second negative clock edge, FF-A toggles again and Q_A changes from 1 to 0.</p> <p>But at this instant Q_A was 1. So $J_B = K_B = 1$ and FF-B will toggle. Hence Q_B changes from 0 to 1.</p> <p>$Q_B Q_A = 10$ after the second clock pulse.</p>
4	After 3rd negative clock edge	<p>On application of the third falling clock edge, FF-A will toggle from 0 to 1 but there is no change of state for FF-B.</p> <p>$Q_B Q_A = 11$ after the third clock pulse.</p>
5	After 4th negative clock edge	On application of the next clock pulse, Q_A will change

		<p>from 1 to 0 as Q_B will also change from 1 to 0.</p> <p>$Q_B Q_A = 00$ after the fourth clock pulse.</p>
--	--	---

Classification of counters

Depending on the way in which the counting progresses, the synchronous or asynchronous counters are classified as follows –

- Up counters
- Down counters
- Up/Down counters

UP/DOWN Counter

Up counter and down counter is combined together to obtain an UP/DOWN counter. A mode control (M) input is also provided to select either up or down mode. A combinational circuit is required to be designed and used between each pair of flip-flop in order to achieve the up/down operation.

- Type of up/down counters
- UP/DOWN ripple counters
- UP/DOWN synchronous counter

UP/DOWN Ripple Counters

In the UP/DOWN ripple counter all the FFs operate in the toggle mode. So either T flip-flops or JK flip-flops are to be used. The LSB flip-flop receives clock directly. But the clock to every other FF is obtained from ($Q = Q$ bar) output of the previous FF.


- **UP counting mode (M=0)** – The Q output of the preceding FF is connected to the clock of the next stage if up counting is to be achieved. For this mode, the mode select input M is at logic 0 (M=0).
- **DOWN counting mode (M=1)** – If M = 1, then the Q bar output of the preceding FF is connected to the next FF. This will operate the counter in the counting mode.

Example

3-bit binary up/down ripple counter.

- 3-bit – hence three FFs are required.
- UP/DOWN – So a mode control input is essential.
- For a ripple up counter, the Q output of preceding FF is connected to the clock input of the next one.
- For a ripple down counter, the Q output of preceding FF is connected to the clock input of the next one.
- For a ripple down counter, the Q bar output of preceding FF is connected to the clock input of the next one.
- Let the selection of Q and Q bar output of the preceding FF be controlled by the mode control input M such that, If M = 0, UP counting. So connect Q to CLK. If M = 1, DOWN counting. So connect Q bar to CLK.

Block Diagram

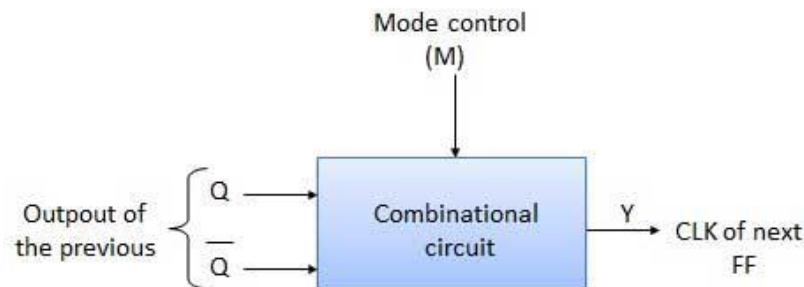

Truth Table

Inputs			Outputs
M	Q	\overline{Q}	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

{ $Y = Q$ for up counter
 { $Y = \overline{Q}$ for up counter

Operation

S.N.	Condition	Operation
1	Case 1 – With $M = 0$ (Up counting mode)	<p>If $M = 0$ and $\overline{M} = 1$, then the AND gates 1 and 3 in fig. will be enabled whereas the AND gates 2 and 4 will be disabled.</p> <p>Hence Q_A gets connected to the clock input of FF-B and Q_B gets connected to the clock input of FF-C.</p> <p>These connections are same as those for the normal up counter. Thus with $M = 0$ the circuit work as an up counter.</p>
2	Case 2: With $M = 1$ (Down counting mode)	<p>If $M = 1$, then AND gates 2 and 4 in fig. are enabled whereas the AND gates 1 and 3 are disabled.</p> <p>Hence $\overline{Q_A}$ gets connected to the clock input of FF-B and $\overline{Q_B}$ gets connected to the clock input of FF-C.</p> <p>These connections will produce a down counter. Thus with $M = 1$ the circuit works as a down counter.</p>

Modulus Counter (MOD-N Counter)

The 2-bit ripple counter is called as MOD-4 counter and 3-bit ripple counter is called as MOD-8 counter. So in general, an n-bit ripple counter is called as modulo-N counter. Where, MOD number = 2^n .

Type of modulus

- 2-bit up or down (MOD-4)
- 3-bit up or down (MOD-8)
- 4-bit up or down (MOD-16)

Application of counters

- Frequency counters
- Digital clock
- Time measurement
- A to D converter
- Frequency divider circuits
- Digital triangular wave generator.

Code: -

```
//JKFF
`timescale 1ns / 1ps

module JKFF(clk,J,K,clr,Q);
input clk,J,K,clr;
output reg Q;

always @(posedge clk)
begin
case({J,K})
2'b00:Q<=Q;
2'b01:Q<=0;
2'b10:Q<=1;
2'b11:Q<=~Q;
endcase
end

always @(posedge clr)
Q<=1'b0;

endmoduler
```



```
//up counter

`timescale 1ns / 1ps

module up_counter(clk,clr,q);

input clk,clr;
output [3:0] q;
wire [3:0] j,k;

assign j[0]=1'b1;
assign k[0]=1'b1;
JKFF FF0(clk,j[0],k[0],clr,q[0]);

assign j[1]=q[0];
assign k[1]=q[0];
JKFF FF1(clk,j[1],k[1],clr,q[1]);

assign j[2]=q[0]&q[1];
assign k[2]=q[0]&q[1];
JKFF FF2(clk,j[2],k[2],clr,q[2]);

assign j[3]=q[0]&q[1]&q[2];
assign k[3]=q[0]&q[1]&q[2];
JKFF FF3(clk,j[3],k[3],clr,q[3]);

endmodule
```

```
//tb
`timescale 1ns / 1ps

module tb_counter();

reg clk,clr;
wire [3:0] q;

up_counter Count(.clk(clk),.clr(clr),.q(q));
//JKFF FF(clk,j,k,clr,q);
initial
begin
clk=1'b0;
forever #3 clk=~clk;
end

initial
begin
clr=1'b1;
#10 clr=1'b0;
#50 clr=1'b1;
#10 clr=1'b0;
end

initial
$monitor($time,"q=%b,clk=%b,clr=%b",q,clk,clr);


initial
#150 $finish;

endmodule
```


Schematics and Simulated Waveforms: -

Schematic:


Up Counter

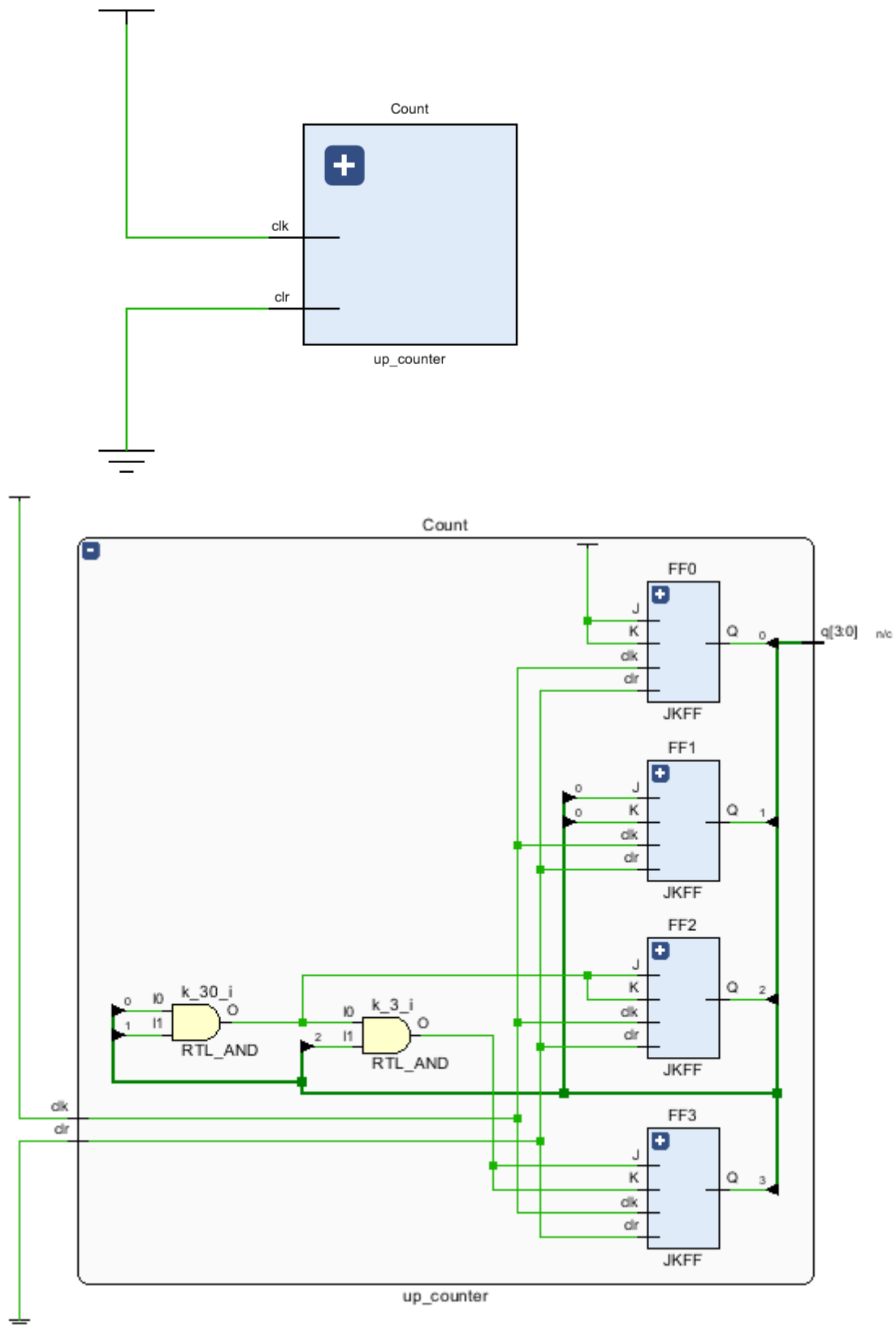

JKFF

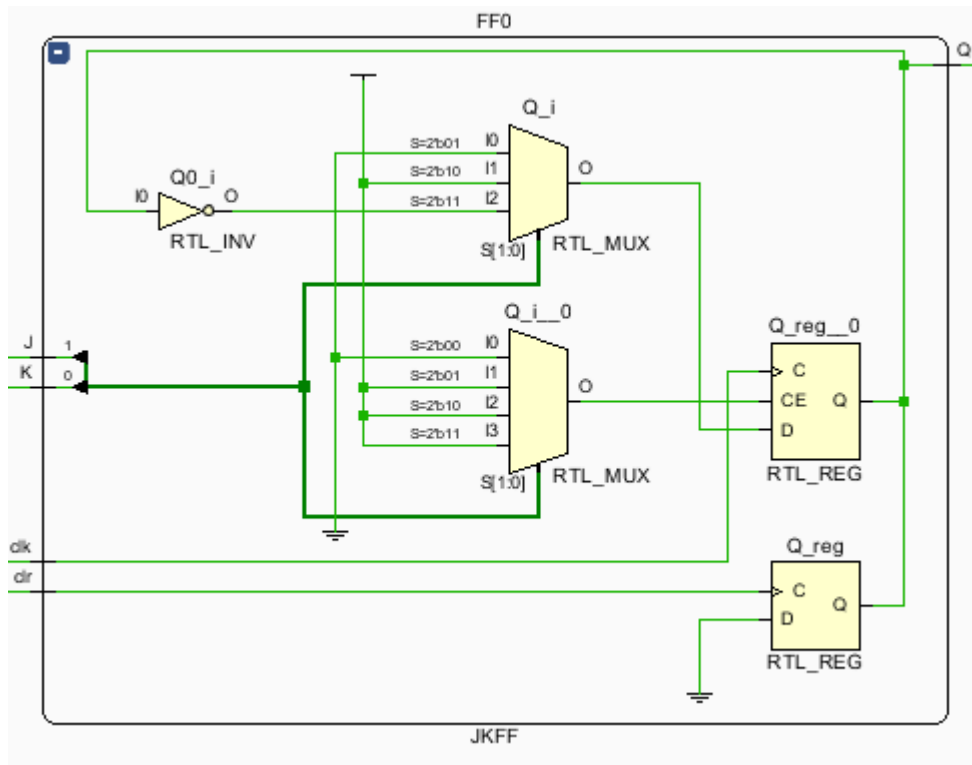

Waveform:

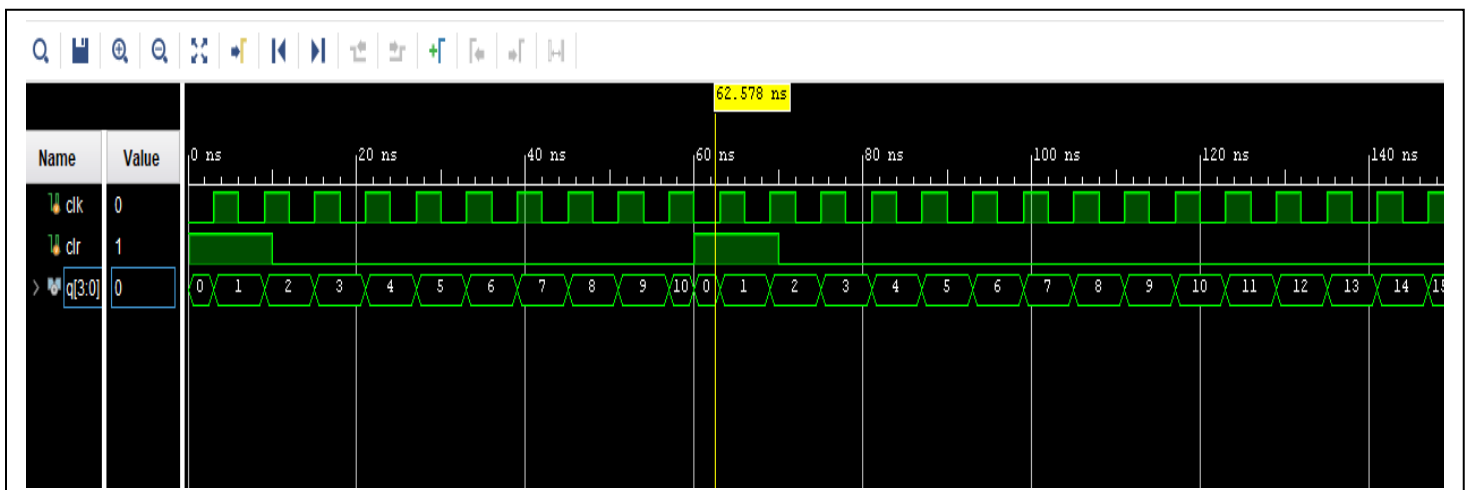

Conclusion: -

Hence , we have successfully designed and simulated Up counter using behavioral modeling style in Verilog HDL. Also verified simulated waveforms with actual truth tables using Xilinx Vivado 2019.1